

EE 105 Lab 03

Bryan Ngo

<2023-03-02 Thu>

Contents

1	DC Simulation Values	1
2	Formatted Plot for AC Magnitude Response	2
3	Parametric Analysis varying the RC Capacitance	2
4	Transient Simulation	4
5	LM741 Simulation	5

1 DC Simulation Values

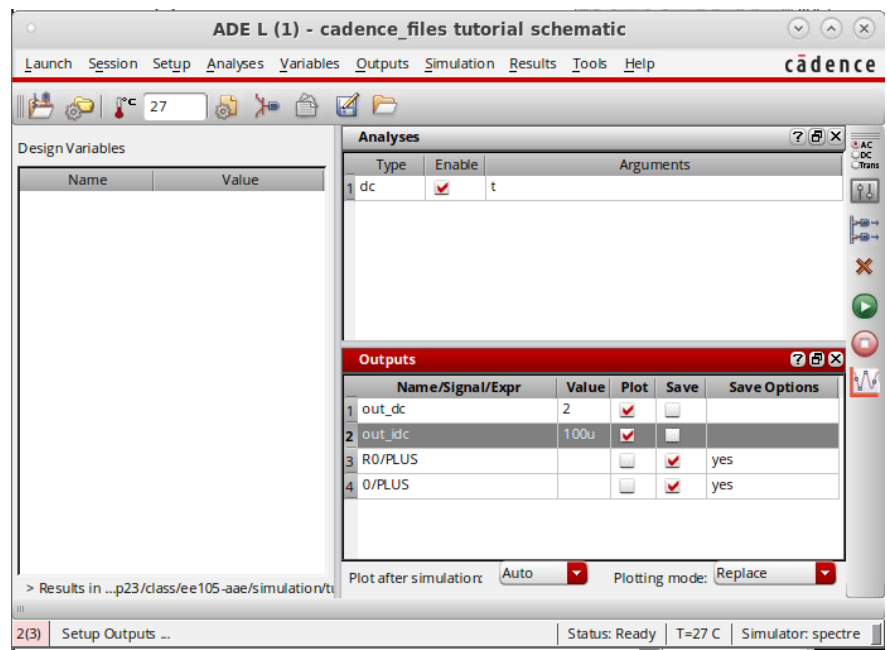


Figure 1: DC simulation parameters.

2 Formatted Plot for AC Magnitude Response

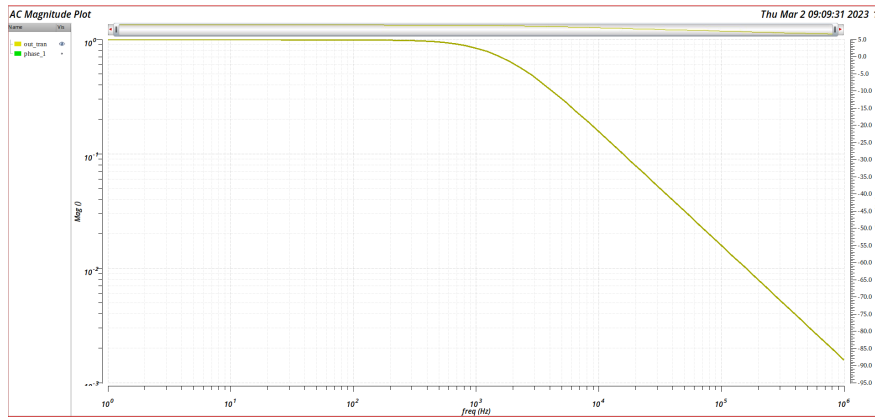


Figure 2: AC magnitude plot.

3 Parametric Analysis varying the RC Capacitance

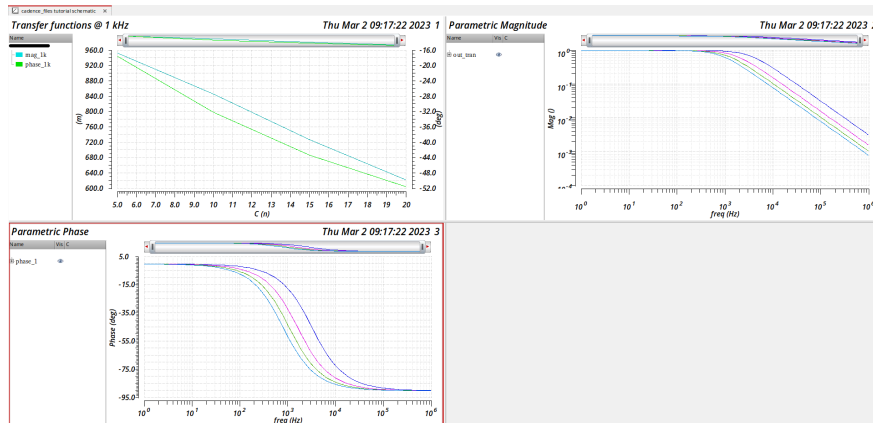


Figure 3: All three plots.



Figure 4: Parametric sweep AC response.

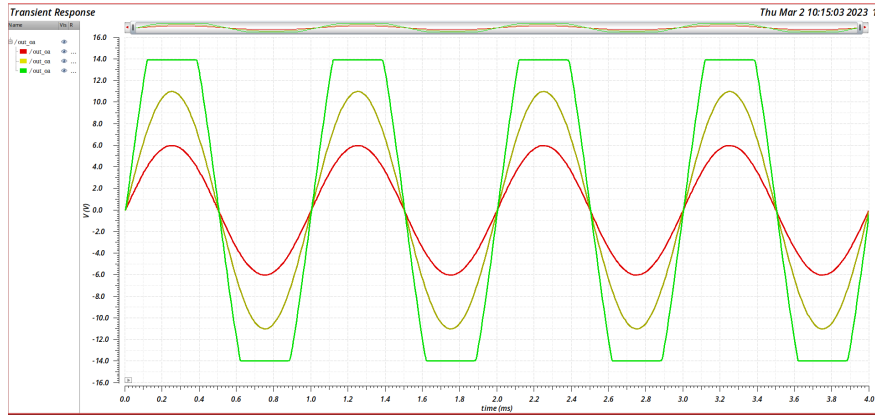


Figure 5: Parametric sweep at 1 kHz.

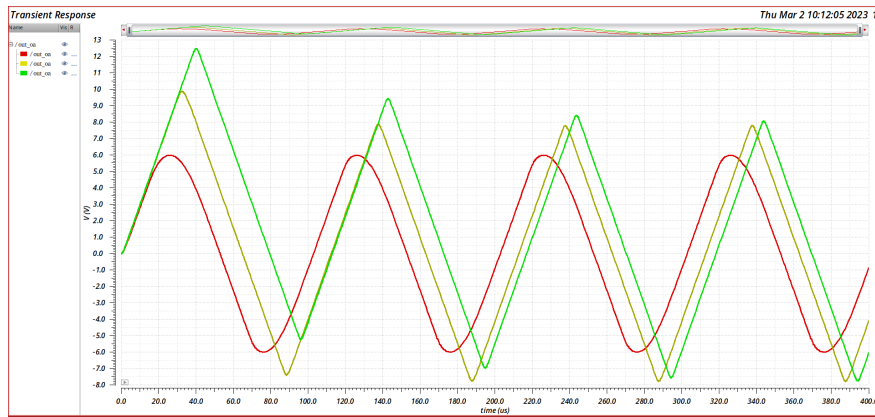


Figure 6: Parametric sweep at 10 kHz.

R [k Ω]	Input Frequency [kHz]	Hand-Calculated Output Amplitude [V]	AC Simulation Output Amplitude [V]	Transient Simulation Output Amplitude [V]	Circuit Output Amplitude [V]
5	1	6	5.999	6	6.55
10	1	11	10.999	11	11.55
20	1	21	20.994	14	14.3
5	10	6	5.990	6	6.55
10	10	11	10.937	8.6	11.5
20	10	21	20.560	8.8	14.3

$$|H(f)| = \frac{1}{\sqrt{1 + (2\pi fRC)^2}} \quad (1)$$

$$\angle H(f) = \tan^{-1}(-2\pi fRC) \quad (2)$$

$$|H(f)|_{C=10\text{ nF}} = 0.85 \quad (3)$$

$$|H(f)|_{C=20\text{ nF}} = 0.62 \quad (4)$$

$$\angle H(f)_{C=10\text{ nF}} = 32.1^\circ \quad (5)$$

$$\angle H(f)_{C=20\text{ nF}} = 51.5^\circ \quad (6)$$

4 Transient Simulation

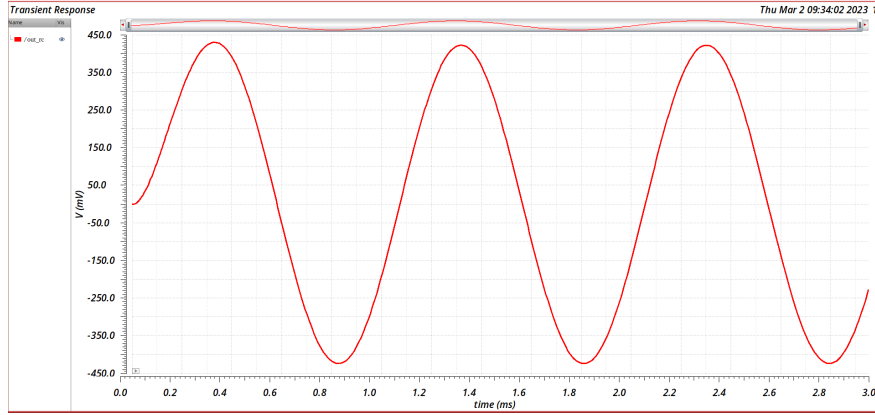


Figure 7: Transient RC simulation.

5 LM741 Simulation

Table 1: Output amplitudes for $R = 5\text{ k}\Omega$. Left: 1 kHz. Right: 10 kHz.

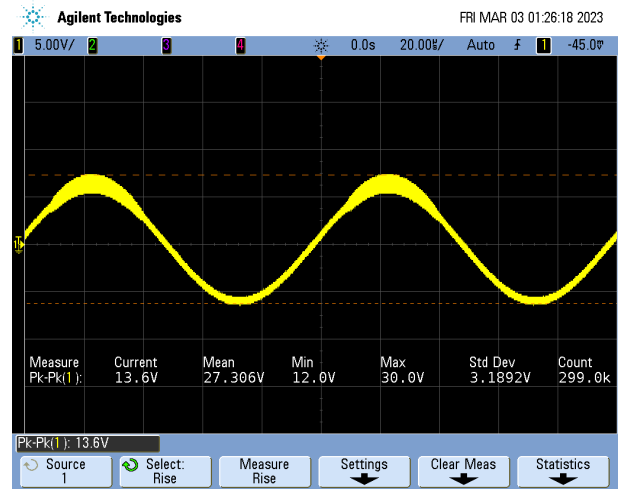
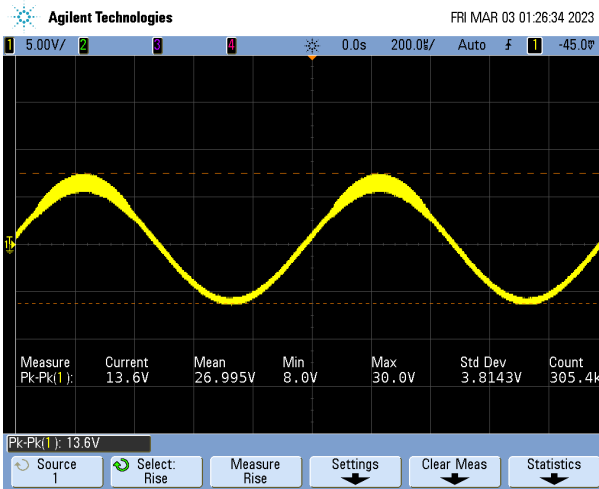


Table 2: Output amplitudes for $R = 10\text{ k}\Omega$. Left: 1 kHz. Right: 10 kHz.


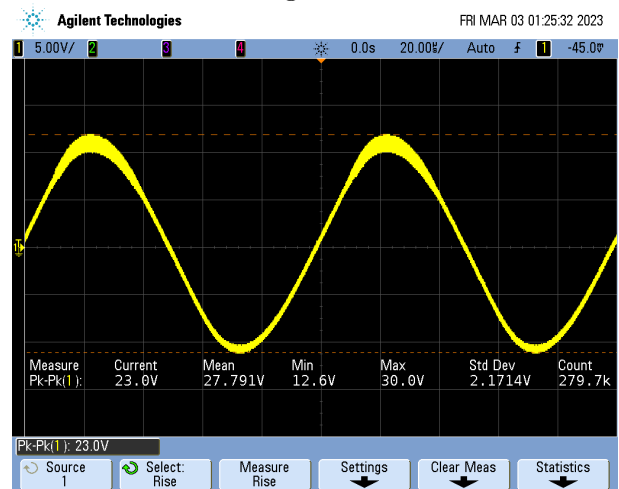
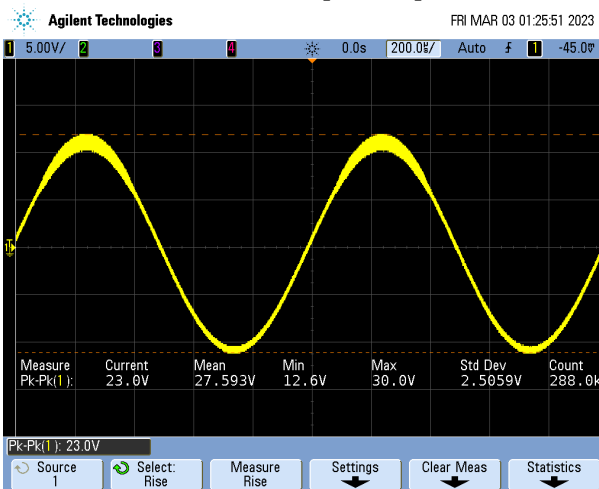


Table 3: Output amplitudes for $R = 20\text{ k}\Omega$. Left: 1 kHz. Right: 10 kHz.

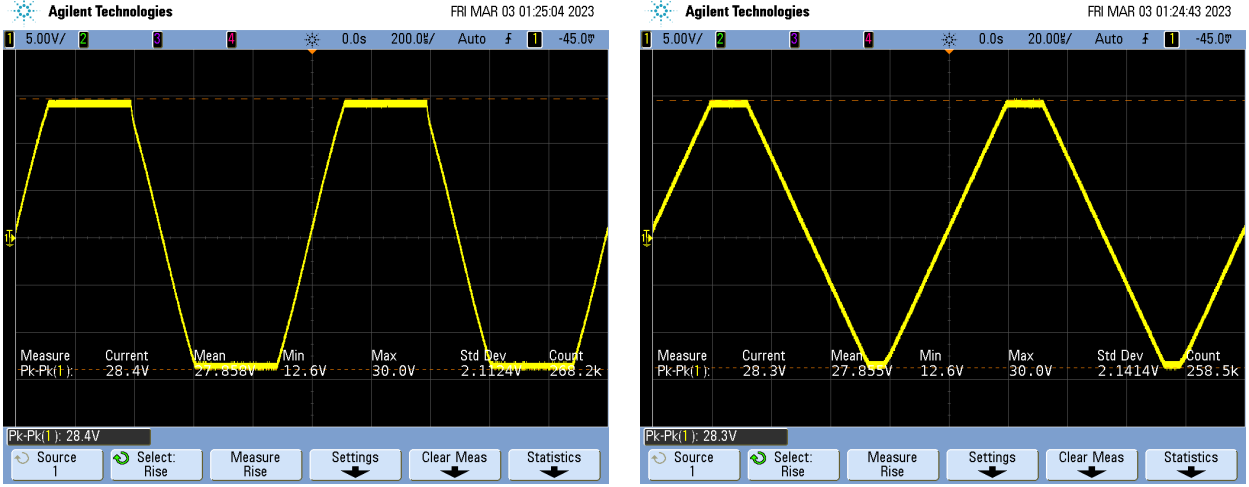

At 1 kHz, the AC simulation had the greatest error. It does not take into account the finite supply voltage.

At 10 kHz, the AC simulation had the greatest error. It does not take into account the slewing of the input signal.

In hand calculation, we assume an ideal op-amp, such as infinite gain and supply voltage, as well as a non-dependence on frequency. In AC simulation, we still maintain infinite supply voltage, but now we have a finite gain and frequency dependence. In transient simulation, we take into account slewing as well as finite supply voltage. This suggests that transient simulation is the closest to reality.