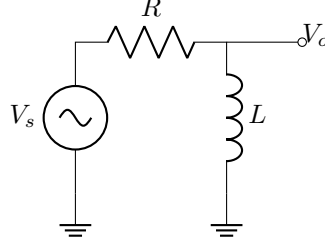


EE 105 HW 02

1



(a) The differential equation governing the circuit is

$$V_s(t) - I_L(t)R - L \frac{dI_L}{dt} = 0 \quad (1)$$

$$\implies \frac{dI_L}{dt} + \frac{R}{L}I_L(t) = \frac{1}{L}V_s(t) \quad (2)$$

The homogeneous solution to the differential equation is

$$I_{L,h}(t) = A_h e^{-\frac{R}{L}t} \quad (3)$$

Assuming the particular solution is of the form $A_p e^{bt}$, we have

$$A_p b e^{bt} + \frac{R}{L} A_p e^{bt} = \frac{1}{L} u(t) \quad (4)$$

Pattern matching, we find that $b = 0$, and $A_p = \frac{1}{R}u(t)$, so our particular solution is

$$I_{L,p}(t) = \frac{1}{R}u(t) \quad (5)$$

The final solution is

$$I_L(t) = I_{L,h}(t) + I_{L,p}(t) = \frac{1}{R}u(t) + A_h e^{-\frac{R}{L}t} \quad (6)$$

$$I_L(0) = 0 = \frac{1}{R} + A_h \implies A_h = -\frac{1}{R}u(t) \quad (7)$$

The final equation is


$$I_L(t) = \frac{1}{R}(1 - e^{-\frac{R}{L}t})u(t) \quad (8)$$

$$V_o(t) = L \frac{dI_L}{dt} = \frac{L}{R}(1 - e^{-\frac{R}{L}t})\delta(t) + e^{-\frac{R}{L}t}u(t) \quad (9)$$

The impulse response, by definition, is

$$h(t) = \frac{d\Phi_o}{dt} = \frac{L}{R}\delta(t) - \frac{R}{L}e^{-\frac{R}{L}t}u(t) = \delta(t) - \frac{R}{L}e^{-\frac{R}{L}t}u(t) \quad (10)$$

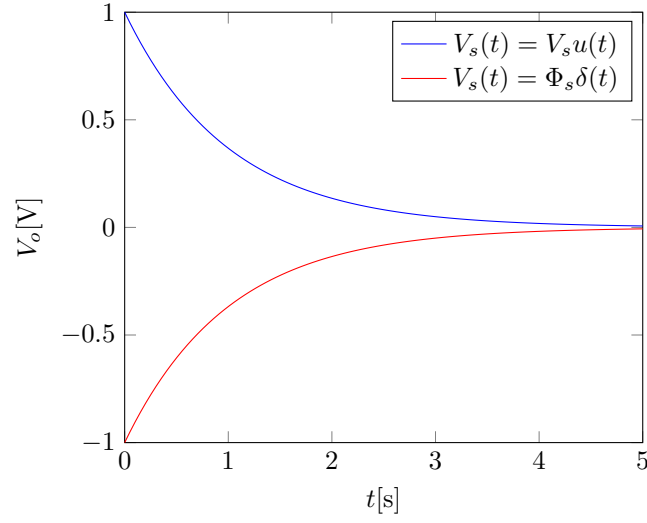Assuming $V_s = 1$ V, $R = 1$ Ω , $L = 1$ H,



(b) Finding the particular solution for the frequency response, we have

$$Abe^{bt} + \frac{R}{L}Ae^{bt} = \frac{1}{L}V_se^{j\omega t} \quad (11)$$

Pattern matching, we find that $b = j\omega$, and $A = \frac{V_s}{R+j\omega L}$. The final equation is

$$I_L(t) = \frac{V_s}{R+j\omega L}e^{j\omega t} \quad (12)$$

$$V_o(t) = L \frac{dI_L}{dt} = \frac{V_s L}{R+j\omega L} j\omega e^{j\omega t} \quad (13)$$

$$= \frac{V_s e^{j\omega t}}{R+j\omega L} (j\omega L) \implies \frac{V_o(t)}{V_s(t)} = \frac{j\omega L}{R+j\omega L} \quad (14)$$

$$\left| \frac{V_o(t)}{V_s(t)} \right| = \frac{\omega L}{\sqrt{R^2 + (\omega L)^2}} \quad (15)$$

$$\angle \frac{V_o(t)}{V_s(t)} = \tan^{-1} \left(\frac{R}{\omega L} \right) \quad (16)$$

This is a high-pass filter since $\lim_{\omega \rightarrow 0} |H(\omega)| = 0$ and $\lim_{\omega \rightarrow \infty} |H(\omega)| = 1$.

2

(a)

$$F(s) = \int_{\mathbb{R}^+} 7t^2 e^{-st} dt \quad (17)$$

By tabular integration, we have

u	v
$7t^2$	e^{-st}
$14t$	$-\frac{1}{s}e^{-st}$
14	$\frac{1}{s^2}e^{-st}$
0	$-\frac{1}{s^3}e^{-st}$

(18)

So the final integral is

$$F(s) = -\frac{7t^2 e^{-st}}{s} - \frac{14te^{-st}}{s^2} - \frac{14e^{-st}}{s^3} \Big|_0^\infty = \frac{14}{s^3} \quad (19)$$

where the integral converges when $\text{Re}\{s\} > 0$.

(b)

$$F(s) = \int_{\mathbb{R}^+} 3e^{-2t} \cos(5t) e^{-st} dt \quad (20)$$

$$= \int_{\mathbb{R}^+} 3e^{-2t} \left(\frac{e^{j5t} + e^{-j5t}}{2} \right) e^{-st} dt \quad (21)$$

$$= \frac{3}{2} \int_{\mathbb{R}^+} e^{(-2-s+5j)t} + e^{(-2-s-5j)t} dt \quad (22)$$

$$= \frac{3}{2} \left(\frac{1}{-2-s+5j} e^{(-2-s+5j)t} + \frac{1}{-2-s-5j} e^{(-2-s-5j)t} \Big|_0^\infty \right) \quad (23)$$

$$= \frac{3}{2} \left(\frac{1}{2+s+5j} + \frac{1}{2+s-5j} \right) \quad (24)$$

$$= \frac{3}{2} \left(\frac{2+s-5j+2+s+5j}{(2+s)^2+25} \right) = 3 \left(\frac{2+s}{(2+s)^2+25} \right) \quad (25)$$

where the integral converges when $\text{Re}\{s\} > 2$.

3

(a)

$$F(s) = \frac{1}{s-1} + \frac{4}{(s-3)^2} + \frac{7}{(s-5)^3} \quad (26)$$

$$= \frac{0!}{(s-1)^1} + \frac{4}{1!} \frac{1!}{(s-3)^2} + \frac{7}{2!} \frac{2!}{(s-5)^3} \quad (27)$$

Using the Laplace transform pair $t^n e^{-\alpha t} \iff \frac{n!}{(s+\alpha)^{n+1}}$, we get

$$f(t) = e^t + 4te^{3t} + \frac{7}{2}t^2 e^{5t} \quad (28)$$

(b)

$$F(s) = \frac{(s+3)+8}{(s+3)^2+4} = \frac{s+3}{(s+3)^2+4} + 4 \frac{2}{(s+3)^2+4} \quad (29)$$

Using the Laplace transform pairs $e^{-\alpha t} \sin(\omega t) \iff \frac{\omega}{(s+\alpha)^2+\omega^2}$ and $e^{-\alpha t} \cos(\omega t) \iff \frac{s+\alpha}{(s+\alpha)^2+\omega^2}$, we get

$$f(t) = e^{-3t} \cos(2t) + 4e^{-3t} \sin(2t) \quad (30)$$

(c)

$$F(s) = \frac{1}{(s+2)(s+4)} = \frac{A}{s+2} + \frac{B}{s+4} \quad (31)$$

$$\implies 1 = A(s+4) + B(s+2) \quad (32)$$


Plugging in $s = -4$ and $s = -2$, we get $A = \frac{1}{2}$ and $B = -\frac{1}{2}$, respectively. We then get

$$F(s) = \frac{1}{2} \frac{1}{s+2} - \frac{1}{2} \frac{1}{s+4} \quad (33)$$


Using the Laplace transform pair $e^{-\alpha t} \iff \frac{1}{s+\alpha}$,

$$f(t) = \frac{1}{2} e^{-2t} - \frac{1}{2} e^{-4t} \quad (34)$$

4

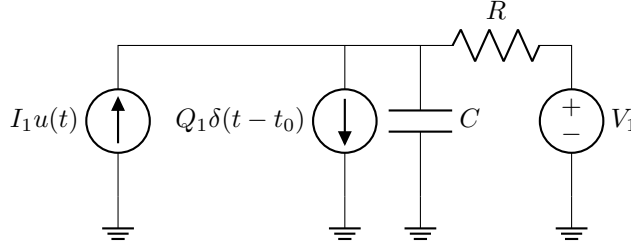

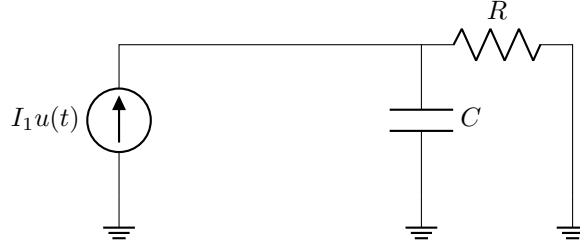Using superposition, we find $V_c(t)$ considering only $I_1 u(t)$:



The initial condition is $V_c(0) = 0$. The homogeneous solution is $V_c(t) = A_h e^{-\frac{t}{RC}}$. The particular solution governing the circuit is


$$\frac{I_1}{C} u(t) = \frac{dV_c}{dt} + \frac{1}{RC} V_c(t) \quad (35)$$

$$\frac{I_1}{C} u(t) = A_p b e^{bt} + \frac{A_p}{RC} e^{bt} \quad (36)$$


$$\implies V_c(t) = I_1 R u(t) \quad (37)$$

$$\implies V_c(t) = I_1 R (1 - e^{-\frac{t}{RC}}) u(t) \quad (38)$$

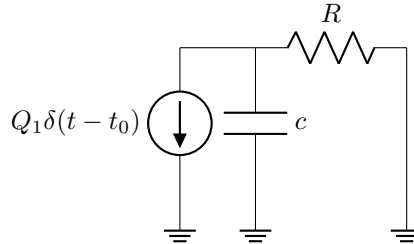Finding $V_c(t)$ considering only $Q_1 \delta(t - t_0)$:



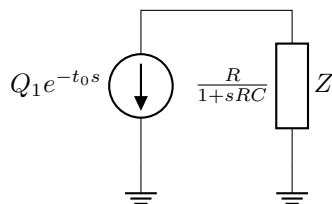
The initial condition is $V_c(t_0) = 0$. Taking the Laplace transform,



By Ohm's law, we get

$$V(s) = -\frac{Q R e^{-t_0 s}}{\frac{1}{RC} + sRC} = -\frac{\frac{Q}{C} e^{-t_0 s}}{\frac{1}{RC} + s} \xrightarrow{\mathcal{L}^{-1}} V_c(t) = -\frac{Q}{C} e^{-\frac{t-t_0}{RC}} u(t-t_0) \quad (39)$$

Finding $V_c(t)$ considering only V_1 :

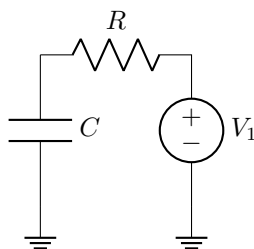

Since V_1 is a constant, $V_c(t) = V_1$ is at steady state. The final equation for the circuit is

$$V_c(t) = I_1 R (1 - e^{-\frac{t}{RC}}) u(t) - \frac{Q}{C} e^{-\frac{t-t_0}{RC}} u(t-t_0) + V_1 \quad (40)$$

Assuming $I_1 = 1$ A, $Q_1 = 1$ C, $C = 1$ F, $R = 1$ Ω , $V_1 = 1$ V, and $t_0 = 2$ s,

