

UNIVERSITY OF CALIFORNIA AT BERKELEY  
College of Engineering  
Department of Electrical Engineering and Computer Sciences  
EE105 Lab Experiments

## Lab 2: Non-Ideal Op-Amps, Pre-Lab Worksheet

Student 1 name: Bryan Ngo

Student 2 name: Kyle Lui


Lab group: Tuesday 8-11 / Tuesday 5-8 / Thursday 8-11 / Thursday 5-8

### 2. Pre-Lab

#### 2.1. Intro to LTSpice

What Resistor value did you use to get a gain of 10? Please attach the plot.

100 k $\Omega$

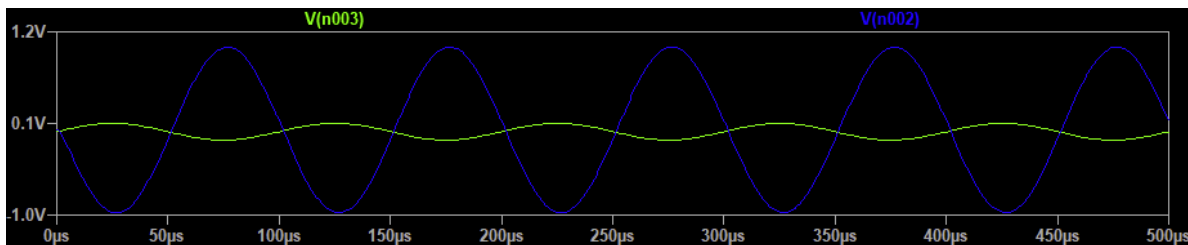

#### 2.2. DC current consumption

Simulated DC current consumption: 79.625 nA



Is it in the range defined in the datasheet? Yes

#### 2.3. DC Open Loop Transfer Characteristic

Open loop gain A<sub>0</sub>: -200 058

Voltage offset V<sub>offset</sub>  $\equiv$  -V<sub>shift</sub>: 1 mV

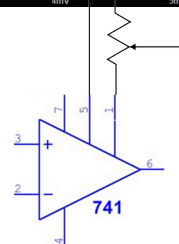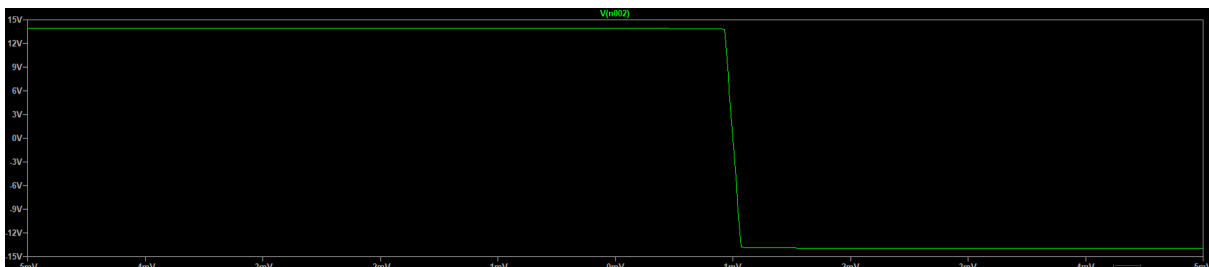Plot of the DC Open Loop Transfer Characteristic:



## 2.4. Nulling the Offset Voltage

Draw the circuit used to null the offset voltage connected to the pinout diagram below:


Why do we use a potentiometer to null the offset voltage? So we can easily adjust our offset voltage to an arbitrary value.

## 2.5. Slew Rate in Unity Gain Configuration

Slew Rate:  $0.33 \text{ V}/\mu\text{s}$

Is it reasonable based on the datasheet? Yes

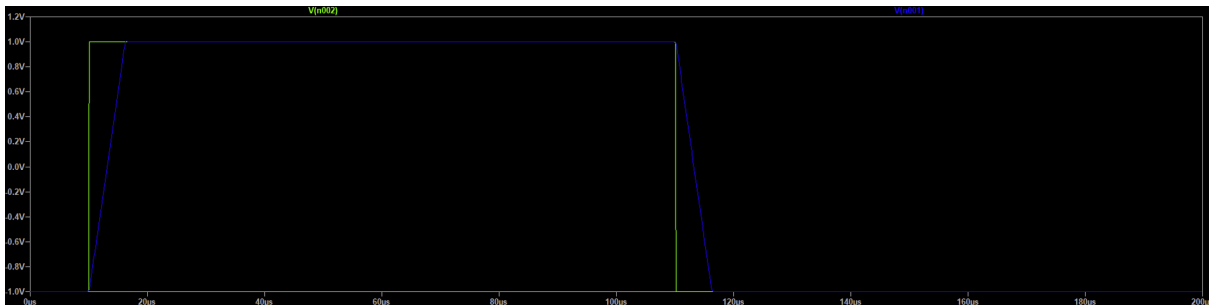Plot of  $V_{out}$  and  $V_{in}$  versus time:




Is the slew rate different for rising and falling voltages? No

## 2.6. Gain and Bandwidth in Unity Gain Configuration

Gain  $A_0$ : 1


Bandwidth  $f_{3dB}$ : 1.54 MHz

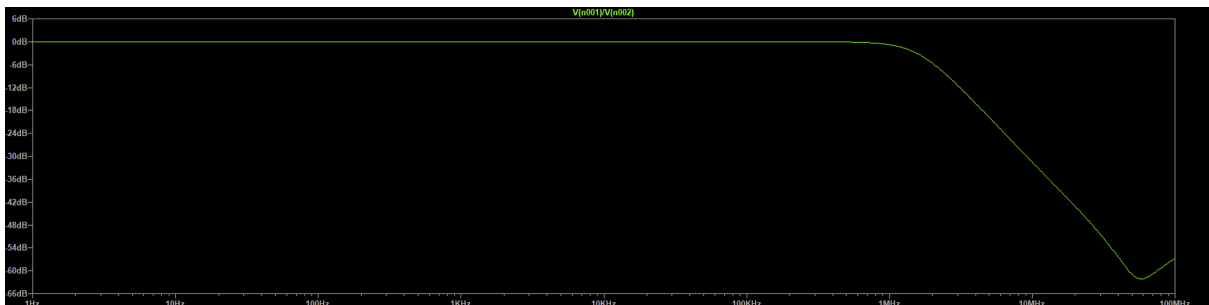Plot of the gain vs frequency (log-log scale):



For 100 KHz input at what amplitude the amplifier will start slewing? 0.5 V

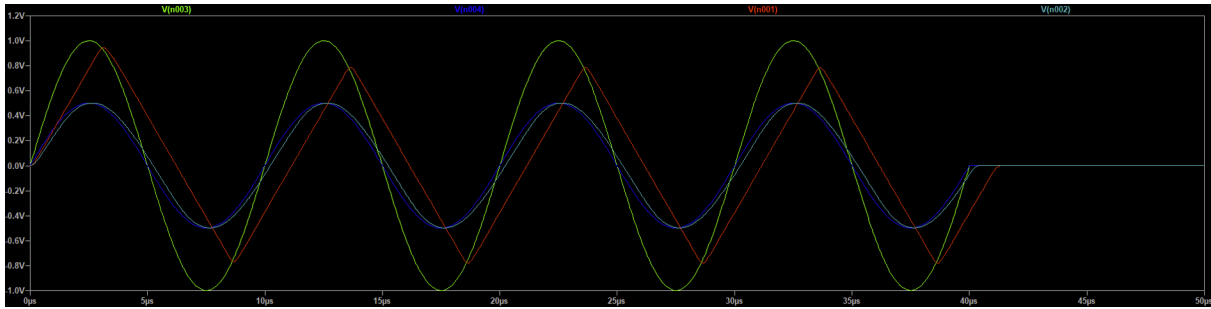
Plot of the input and the output for this amplitude, and for twice this amplitude, at the same plot:



## 2.7. Gain and Bandwidth in Non-Inverting Amplifier Configuration

R=10kΩ	Gain A0: 10
	Bandwidth f3dB: 110 kHz
R=100kΩ	Gain A0: 100
	Bandwidth f3dB: 10 kHz

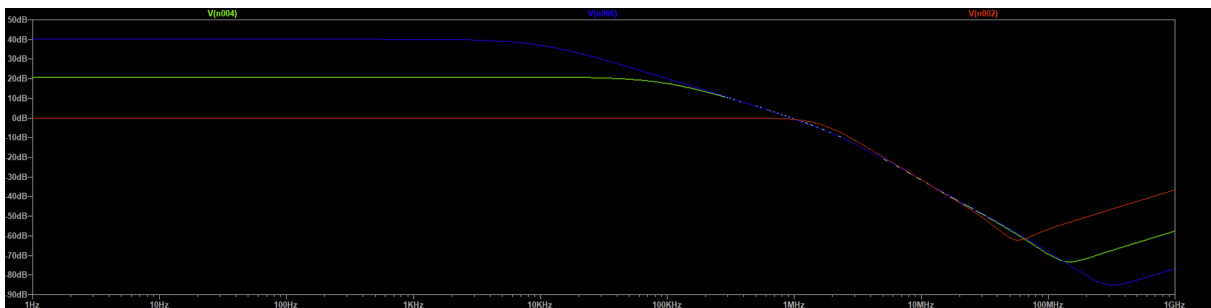Plot of magnitude response of the voltage gain in log-log scale for the two non-inverting amplifier circuits and the circuit from Problem 2.6 on the same plot:



At approximately what frequency and gain do the three curves intersect on the plot? What does this mean? **10 MHz. This point can be interpreted as the point at which all the circuits have the same signal energy/power, since the magnitude of the signals are all equal here.**

With R=10kΩ, for 10KHz input at what amplitude the amplifier will start slewing? **0.5 V**

Plot of the input and the output for this amplitude, and for twice this amplitude, at the same plot:

