

Experiment 1: Non-Ideal Op-Amps, Lab Report

Student 1 name: [Bryan Ngo](#)

Student 2 name: [Kyle Lui](#)

Lab group: Monday 11-2 / Monday 2-5 / Monday 5-8 / Wednesday 9-12 / [Thursday 8-11](#)

3. Lab

3.1. DC current consumption

Measured DC current consumption: [1.3 mA](#)

Is it in the range defined in the datasheet? [No](#)


3.2. DC Open Loop Transfer Characteristic

Measured values of attenuator resistors: [100.2 k \$\Omega\$](#) , [98.2 \$\Omega\$](#)

Open loop gain A_0 : [11 672](#)

Voltage offset $V_{\text{offset}} \equiv -V_{\text{shift}}$: [0.83 V](#)

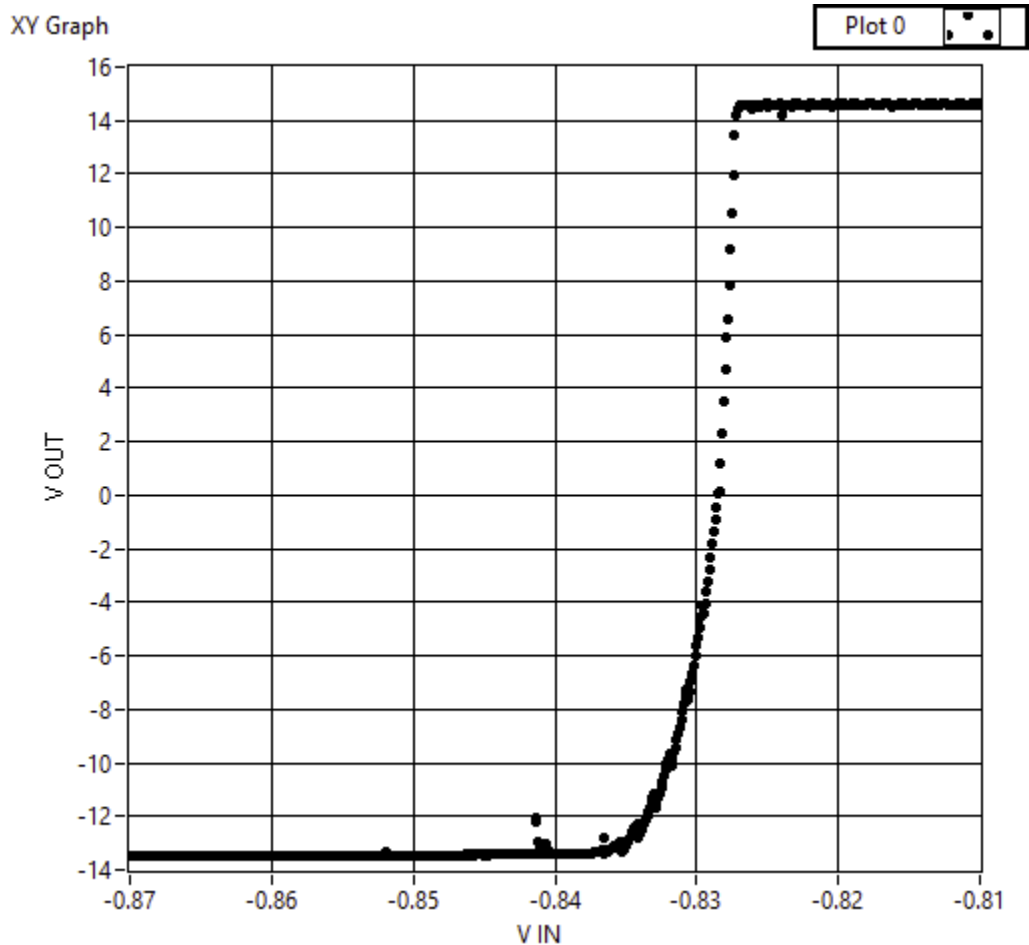Plot of the DC Open Loop Transfer Characteristic:



3.3. Nulling the Offset Voltage

The resistance from -15V to pin1 of the opamp: **4.1 k Ω**

The resistance from -15V to pin5 of the opamp: **6.5 k Ω**

3.4. Slew Rate in Unity Gain Configuration

Rising Slew Rate: **0.75 V/ μ s**

Falling Slew Rate: **0.65 V/ μ s**




Is it reasonable based on the datasheet? **Yes**

Oscilloscope trace(s) of the slew rate measurements:

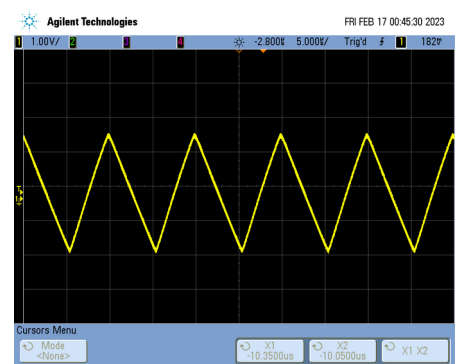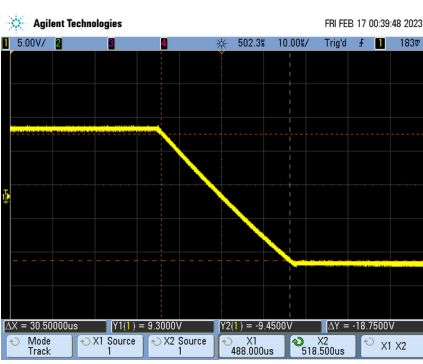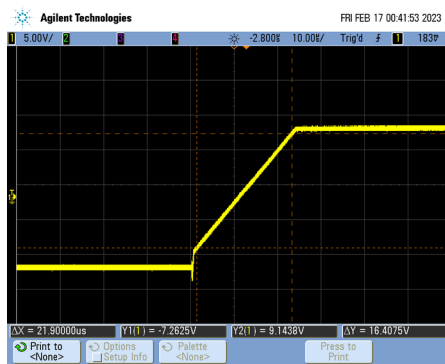3.5. Gain and Bandwidth in Unity Gain Configuration

Based on your slew rate measurements, for 100KHz input at what amplitude the amplifier will start slewing? **1.2 V rising, 1 V falling**

Oscilloscope trace of the slewing output sine signal when doubling this amplitude:



Gain A0: **1.06**

Bandwidth f3dB: **800 kHz**

3.6. Gain and Bandwidth in Non-Inverting Amplifier Configuration

| | |
|-----------------|------------------------|
| R=10k Ω | Gain A0: 11 |
| | Bandwidth f3dB: 75 kHz |
| R=100k Ω | Gain A0: 109 |
| | Bandwidth f3dB: 10 kHz |

Plot of magnitude response of the voltage gain in dB for the two non-inverting amplifier circuits and the circuit from Problem 3.5 on the same plot:

Magnitude Response

