
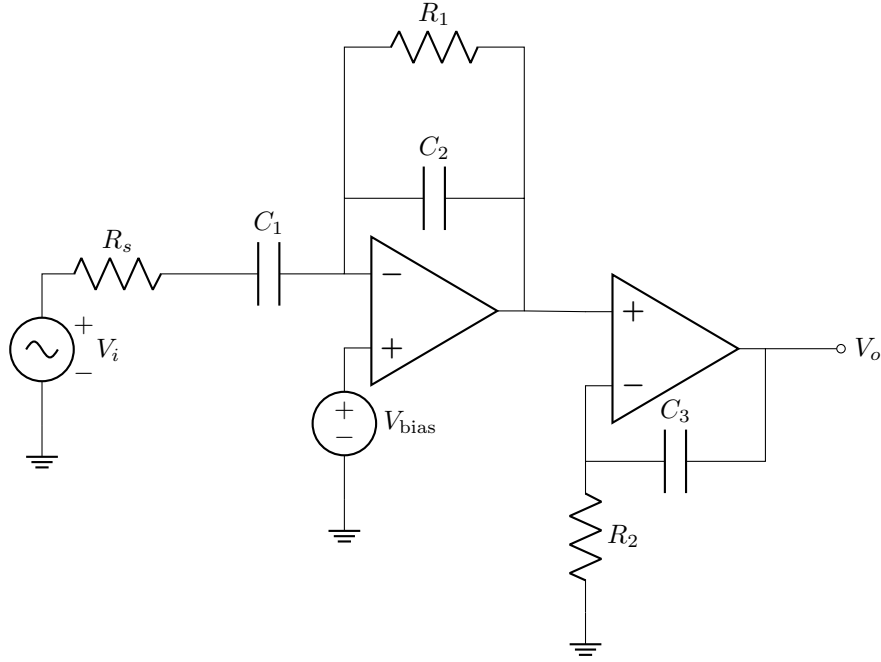


EE 105 HW 05

1

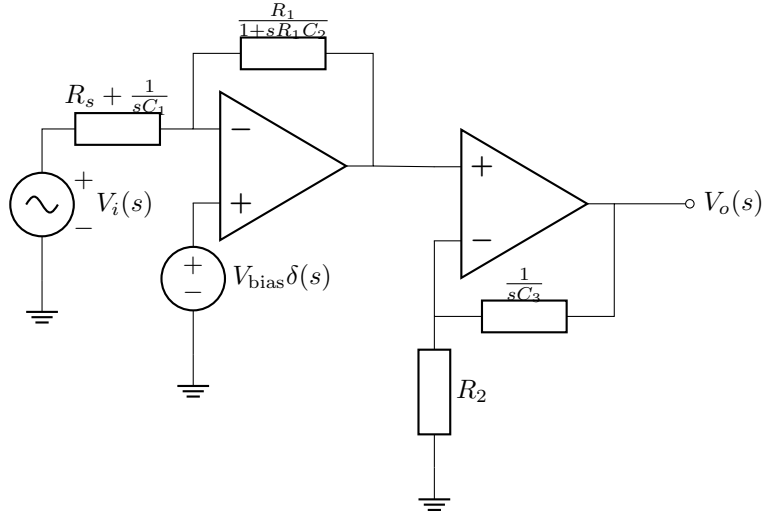

In the s -domain,



Using superposition, we can derive the output of the first op-amp as

$$V_x(s) = -V_i(s) \frac{\frac{R_1}{1+sR_1C_2}}{\frac{1+sR_1C_2}{1+sR_sC_1} + \frac{1}{sC_1}} + V_{\text{bias}}\delta(s) \left(1 + \frac{\frac{R_1}{1+sR_1C_2}}{\frac{1+sR_1C_2}{1+sR_sC_1} + \frac{1}{sC_1}} \right) \quad (1)$$

$$= -V_i(s) \frac{sR_1C_1}{(1+sR_1C_2)(1+sR_sC_1)} + V_{\text{bias}}\delta(s) \left(1 + \frac{sR_1C_1}{(1+sR_1C_2)(1+sR_sC_1)} \right) \quad (2)$$


We can then multiply by the second op-amp's transfer function to get

$$V_o(s) = V_x \left(1 + \frac{1}{sR_2C_3} \right) \quad (3)$$

$$= \left(-V_i(s) \frac{sR_1C_1}{(1 + sR_1C_2)(1 + sR_sC_1)} + V_{\text{bias}}^0(s) \left(1 + \frac{sR_1C_1}{(1 + sR_1C_2)(1 + sR_sC_1)} \right) \right) \left(1 + \frac{1}{sR_2C_3} \right) \quad (4)$$


$$\Rightarrow \frac{V_o(s)}{V_i(s)} = -\frac{sR_1C_1}{(1 + sR_1C_2)(1 + sR_sC_1)} \left(1 + \frac{1}{sR_2C_3} \right) \quad (5)$$

2

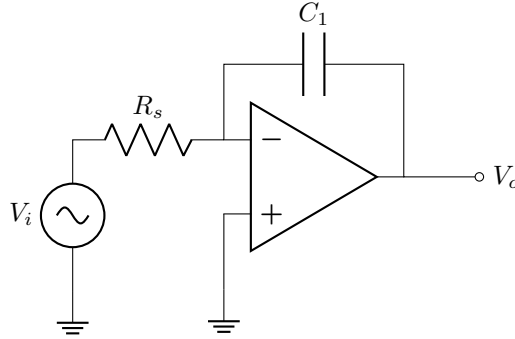

- (a) Applying a test voltage at the input, the current through R_s is $I_{test} = \frac{V_{test} - V^-}{R_s}$, where we use the ideality of the op amp to cancel out V^- . This means that $Z_{test} = \frac{V_{test}}{I_{test}} = R_s$. Applying a test voltage at the output, since we are applying a DC source, the voltage difference at the capacitor is 0 due to the virtual short, therefore we have $Z_{out} = 0$.

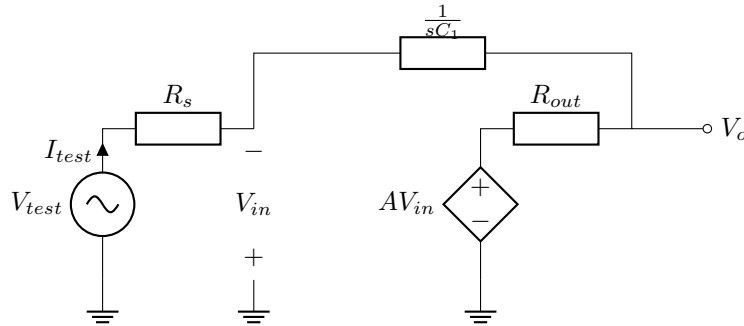- (b) The circuit in the s -domain is now




We can create the loop equation

$$V_{test} - I_{test}R_s - I_{test}\frac{1}{sC_1} - I_{test}R_{out} + A(V_{test} - I_{test}R_s) = 0 \quad (6)$$

$$V_{test}(1 + A) - I_{test} \left(R_s + \frac{1}{sC_1} - R_{out} - AR_s \right) = 0 \quad (7)$$

$$Z_{in} = \frac{V_{test}}{I_{test}} = \frac{R_s + \frac{1}{sC_1} - R_{out} - AR_s}{1 + A} \quad (8)$$

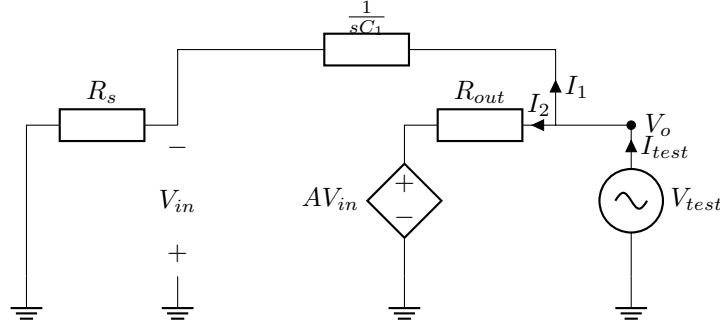For the output impedance, we can apply a test voltage at V_o and null V_i to get



We can obtain the node equations

$$I_{test} = \frac{V_{test} - AV_{in}}{R_{out}} + sC_1(V_{test} + V_{in}) \quad (9)$$

$$V_{in} = V_{test} - sR_s C_1(V_{test} + V_{in}) \quad (10)$$

$$\Rightarrow V_{in} = V_{test} \frac{1 - sR_s C_1}{1 + sR_s C_1} \quad (11)$$


$$I_{test} = V_{test} \left(\frac{1}{R_{out}} - \frac{A}{R_{out}} \frac{1 - sR_s C_1}{1 + sR_s C_1} + sC_1 \left(1 + \frac{1 - sR_s C_1}{1 + sR_s C_1} \right) \right) \quad (12)$$

$$\Rightarrow \frac{1}{Z_{out}} = \left(\frac{1}{R_{out}} - \frac{A}{R_{out}} \frac{1 - sR_s C_1}{1 + sR_s C_1} + sC_1 \left(1 + \frac{1 - sR_s C_1}{1 + sR_s C_1} \right) \right) \quad (13)$$

When $A \rightarrow \infty$, we have $G_{out} = \infty \Rightarrow Z_{out} = 0$ and $Z_{in} = R_s$.

(c) The answer can be obtained similarly by substituting the constant gain A with the gain $\frac{A}{1+j\frac{\omega}{\omega_0}}$.

3

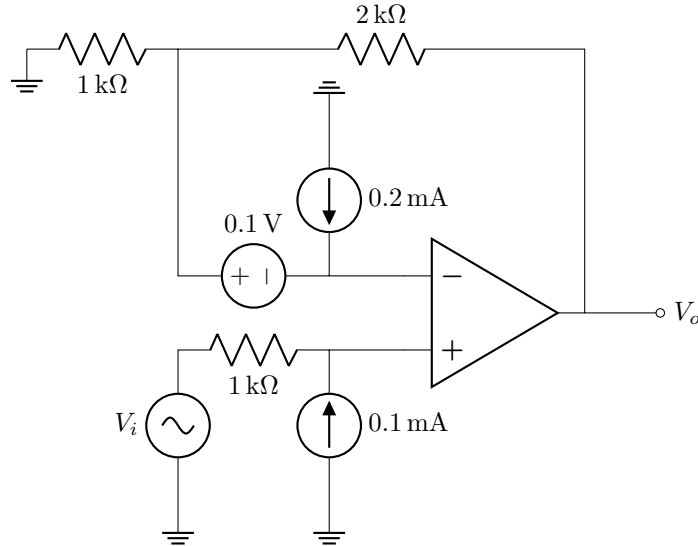

Slew rate: $2 \text{ V } \mu\text{s}^{-1}$

Signal:

$$x(t) = \begin{cases} 1 \text{ V} & 0 \leq t \leq 4 \mu\text{s} \\ 0 & \text{elsewhere} \end{cases} \quad (14)$$

We can define the node equations

$$0.2 \text{ mA} = \frac{V^- + 0.1 \text{ V} - V_o}{2 \text{ k}\Omega} + \frac{V^- + 0.1 \text{ k}\Omega}{1 \text{ k}\Omega} \quad (15)$$


$$V_i + (0.1 \text{ mA})(1 \text{ k}\Omega) = V^+ \quad (16)$$

$$V^+ = V^- \quad (17)$$

$$\Rightarrow 0.2 \text{ mA} = \frac{V_i + 0.1 \text{ V} + 0.1 \text{ V} - V_o}{2 \text{ k}\Omega} + \frac{V_i + 0.1 \text{ V} + 0.1 \text{ V}}{1 \text{ k}\Omega} \quad (18)$$

$$0.4 \text{ V} = V_i + 0.2 \text{ V} - V_o + 2V_i + 0.4 \text{ V} \quad (19)$$
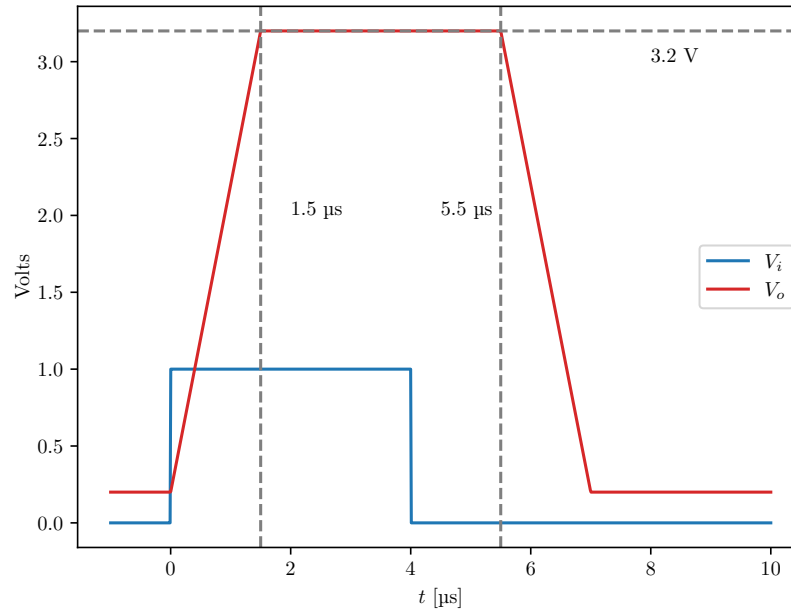
$$\Rightarrow V_o = 3V_i + 0.2 \text{ V} \quad (20)$$



4

$$V_{cm} = \frac{V_1 + V_2}{2} \quad (21)$$

$$V_d = V_2 - V_1 \quad (22)$$

$$V_{out} = A_{cm}V_{cm} + A_dV_d \quad (23)$$

We can solve for V_1 and V_2 in terms of V_{cm} and V_d as

$$V_1 = V_{cm} - \frac{V_d}{2} \quad (24)$$

$$V_2 = V_{cm} + \frac{V_d}{2} \quad (25)$$

Then, we can find V_{out} as

$$V_{out} = -\frac{\overset{10}{\cancel{R_2}}}{\cancel{R_1}} V_1 + \left(1 + \frac{\overset{10}{\cancel{R_2}}}{\cancel{R_1}}\right) \left(\frac{R_4}{R_2 + R_4}\right) V_2 \quad (26)$$

$$= -10V_1 + 11 \left(1 + \frac{\overset{\frac{10}{11}}{\cancel{R_2}}}{\cancel{R_4}}\right) V_2 = -10V_1 + 10V_2 \quad (27)$$

$$= -10 \left(\cancel{V_{cm}} - \frac{V_d}{2}\right) + 10 \left(\cancel{V_{cm}} + \frac{V_d}{2}\right) = 10V_d \quad (28)$$

So $A_{cm} = 0$ and $A_d = 10$.