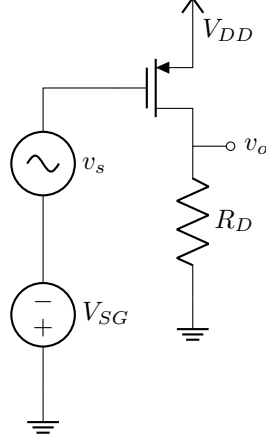


EE 105 HW 08

1




- (a) We have that $V_{SG} - |V_{TP}| = V_0$ and that $\mu_0 C_{ox} \frac{W}{L} = k$. For the PMOS to be in saturation mode, we want

$$V_{SD} \leq V_0 = V_{DD} - I_D R_D \quad (1)$$

$$\Rightarrow R_D = \frac{V_{DD} - V_0}{I_D} = \frac{2(V_{DD} - V_0)}{kV_0^2} \quad (2)$$

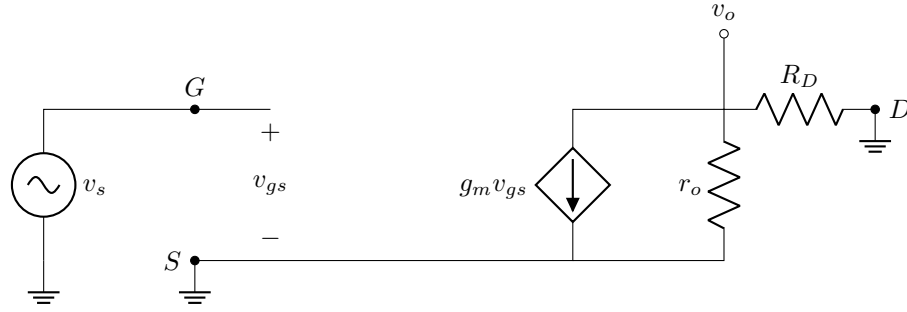- (b) Converting to an NMOS common-source amplifier, the small-signal equivalent is




We then have

$$g_m v_s = \frac{-v_o}{r_o \parallel R_D} \quad (3)$$

$$g_m (r_o \parallel R_D) v_s = -v_o \quad (4)$$

$$\Rightarrow A = \frac{v_o}{v_s} = -g_m \frac{r_o R_D}{r_o + R_D} \quad (5)$$

2

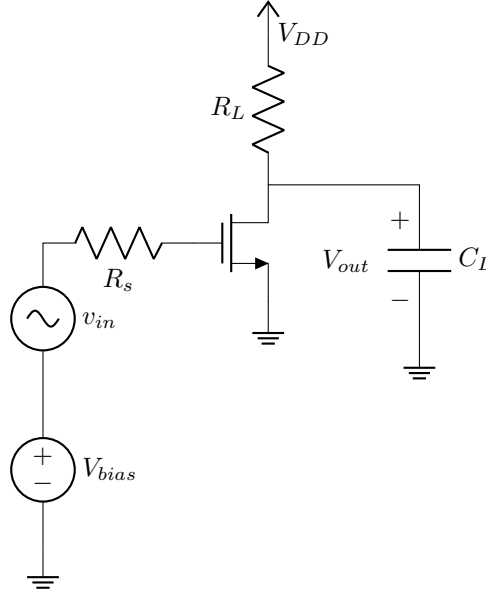

$$I_{DS} = k(V_{GS} - V_{TH})^2 \quad (6)$$

$$V_{TH} = 0.65 \text{ V} \quad (7)$$

$$k = 20 \text{ mA V}^{-2} \quad (8)$$

(a)

$$V_{DD} = 1.8 \text{ V} \quad (9)$$

$$R_s = 10 \text{ k}\Omega \quad (10)$$

$$R_L = 1 \text{ k}\Omega \quad (11)$$

$$C_L = 1 \text{ pF} \quad (12)$$

$$V_{bias} = 0.85 \text{ V} \quad (13)$$

At the DC operating point, we have $v_s = 0$, so we have

$$V_{GS} = V_{bias} = 0.85 \text{ V} \quad (14)$$


$$I_{DS} = k(V_{bias} - 0.65 \text{ V})^2 = 0.8 \text{ mA} \quad (15)$$

$$V_{out} = V_{DD} - I_{DS}R_L = 1 \text{ V} \quad (16)$$

(b)

$$g_m = \frac{\partial I_{DS}}{\partial V_{GS}} = 2k(V_{GS} - V_{TH}) = 8 \text{ mS} \quad (17)$$

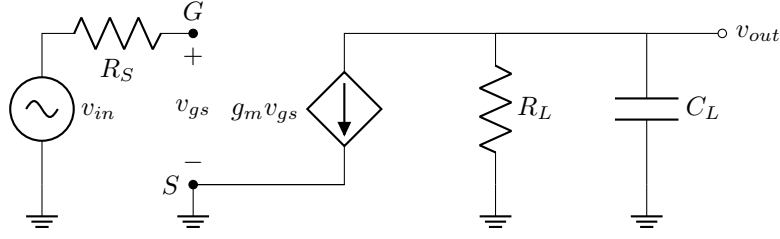(c) The small-signal model of the circuit is



The transfer function is

$$g_m v_{in} + \frac{v_{out}}{R_L} + sC_L v_{out} = 0 \quad (18)$$

$$g_m v_{in} = -v_{out} \left(\frac{1}{R_L} + sC_L \right) \quad (19)$$

$$\Rightarrow \frac{v_{out}}{v_{in}} = -\frac{g_m R_L}{1 + sR_L C_L} \quad (20)$$


(d)

$$\lim_{\omega \rightarrow 0} |H(j\omega)| = g_m R_L = 8 \quad (21)$$

$$|H(j\omega)| = \frac{g_m R_L}{\sqrt{1 + (R_L C_L)^2}} \quad (22)$$

$$\Rightarrow \omega_c = \frac{g_m R_L}{2\pi R_L C_L} = 1.27 \text{ GHz} \quad (23)$$

3

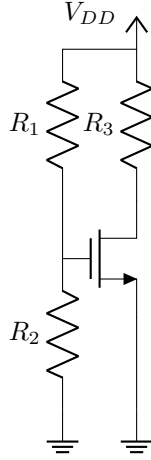

$$V_{DD} = 3.3 \text{ V} \quad (24)$$

$$R_1 = 2.3 \text{ k}\Omega \quad (25)$$

$$R_2 = 1.2 \text{ k}\Omega \quad (26)$$

$$R_3 = 1.2 \text{ k}\Omega \quad (27)$$

$$V_{TH} = 0.5 \text{ V} \quad (28)$$

$$\lambda = 0 \text{ V}^{-1} \quad (29)$$

$$\mu_n C_{ox} = 2 \times 10^{-4} \text{ A V}^{-2} \quad (30)$$

$$\frac{W}{L} = 20 \quad (31)$$

$$L = 0.5 \mu\text{m} \quad (32)$$


- (a) The gate voltage forms a resistive divider, so we have $V_{GS} = 1.13 \text{ V}$. Since $V_{GS} > V_{TH}$, the NMOS is either in the linear/triode or saturation region. We can test the saturation condition for an NMOS:

$$V_{DS} = V_{DD} - I_D R_D \geq V_{GS} - V_{TH} \quad (33)$$

$$\Rightarrow R_D \leq \frac{V_{DD} + V_{TH} - V_{GS}}{I_D} = \frac{2(V_{DD} + V_{TH} - V_{GS})}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2} = 3.3 \text{ k}\Omega > R_3 \quad (34)$$

Since the condition is satisfied, the NMOS is in saturation mode. Thus, $V_{DS} = V_{DD} - I_D R_D = 2.34 \text{ V}$. This confirms the operating region.

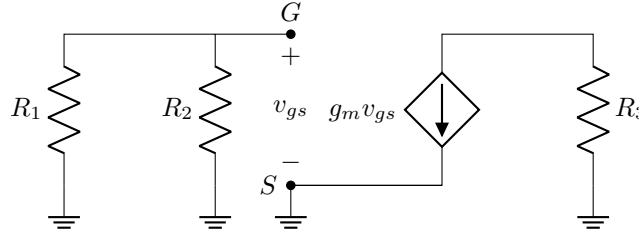
- (b) Since $\lambda = 0 \text{ V}^{-1}$, there is no channel-length modulation, so $r_o = \infty$. The small-signal model is



We can find g_m as

$$g_m = \frac{\partial I_D}{\partial V_{DS}} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) = 2.52 \text{ mS} \quad (35)$$

- (c) The small-signal model is now

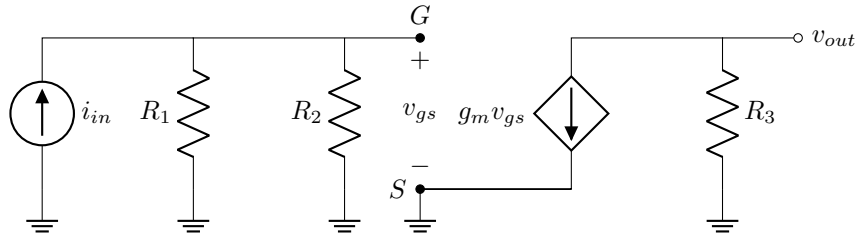

We have the equation

$$-v_{out} = g_m i_{in} (R_1 \parallel R_2) R_3 \Rightarrow A = \frac{v_{out}}{i_{in}} = -g_m (R_1 \parallel R_2) R_3 = -2.39 \text{ k}\Omega \quad (36)$$

4

$$\begin{aligned}
V_{GS} &= 1 \text{ V} \\
V_{DS} &= 1 \text{ V} \\
V_{SB} &= 0.2 \text{ V} \\
V_{TN} &= 0.5 \text{ V} \\
W &= 5 \mu\text{m} \\
L &= 1 \mu\text{m} \\
t_{ox} &= 10 \text{ nm} \\
\epsilon_{ox} &= 3.9\epsilon_0 \\
L_j &= 2 \mu\text{m} \\
L_{ov} &= 0.05 \mu\text{m} \\
C_{j0} &= 1 \text{ mF m}^{-2} \\
C_{j,sw0} &= 4 \times 10^{-10} \text{ F m}^{-1} \\
\phi_b &= 1 \text{ V} \\
C_{\text{fringe}} &= 1 \text{ fF}
\end{aligned}$$

$$C_{gs} = \frac{2}{3} W L C_{ox} + C_{ov} = \frac{2}{3} W L \frac{\epsilon_{ox}}{t_{ox}} + L_{ov} W \frac{\epsilon_{ox}}{t_{ox}} = 1.24 \times 10^{-14} \text{ F} \quad (37)$$

$$C_{gd} = C_{ov} + C_{\text{fringe}} = L_{ov} W C_{ox} + C_{\text{fringe}} = 1.86 \times 10^{-15} \text{ F} \quad (38)$$

$$A_{d,j} = A_{s,j} = L_j W = 1 \times 10^{-11} \text{ m}^2 \quad (39)$$

$$P_{d,j} = P_{s,j} = 2L_j + W = 9 \mu\text{m} \quad (40)$$

$$C_{db} = \frac{C_{j0}}{\sqrt{1 + \frac{V_{DB}}{\phi_B}}} A_{d,j} + \frac{C_{j,sw0}}{\sqrt{1 + \frac{V_{DB}}{\phi_B}}} P_{d,j} = 1.01 \times 10^{-14} \text{ F} \quad (41)$$

$$C_{sb} = \frac{C_{j0}}{\sqrt{1 + \frac{V_{SB}}{\phi_B}}} A_{s,j} + \frac{C_{j,sw0}}{\sqrt{1 + \frac{V_{SB}}{\phi_B}}} P_{s,j} = 1.24 \times 10^{-14} \text{ F} \quad (42)$$