

Experiment 5: MOSFET Characterization

Lab Report

Student 1 name: [Bryan Ngo](#)

Student 2 name: [Kyle Lui](#)

Lab group: Tuesday 8-11 / Tuesday 5-8 / [Thursday 8-11](#) / Thursday 5-8

3. Lab


3.1. MOSFET Characterization

Using Python/Matlab, find V_T , K_p , and channel length modulation (λ) of the transistor. You can use curve fitting packages/toolboxes.


$$V_T = 2 \text{ V}$$

$$K_p = 0.16 \text{ } \Omega \text{ V}^{-1}$$


$$\lambda = -0.12 \text{ V}^{-1}$$

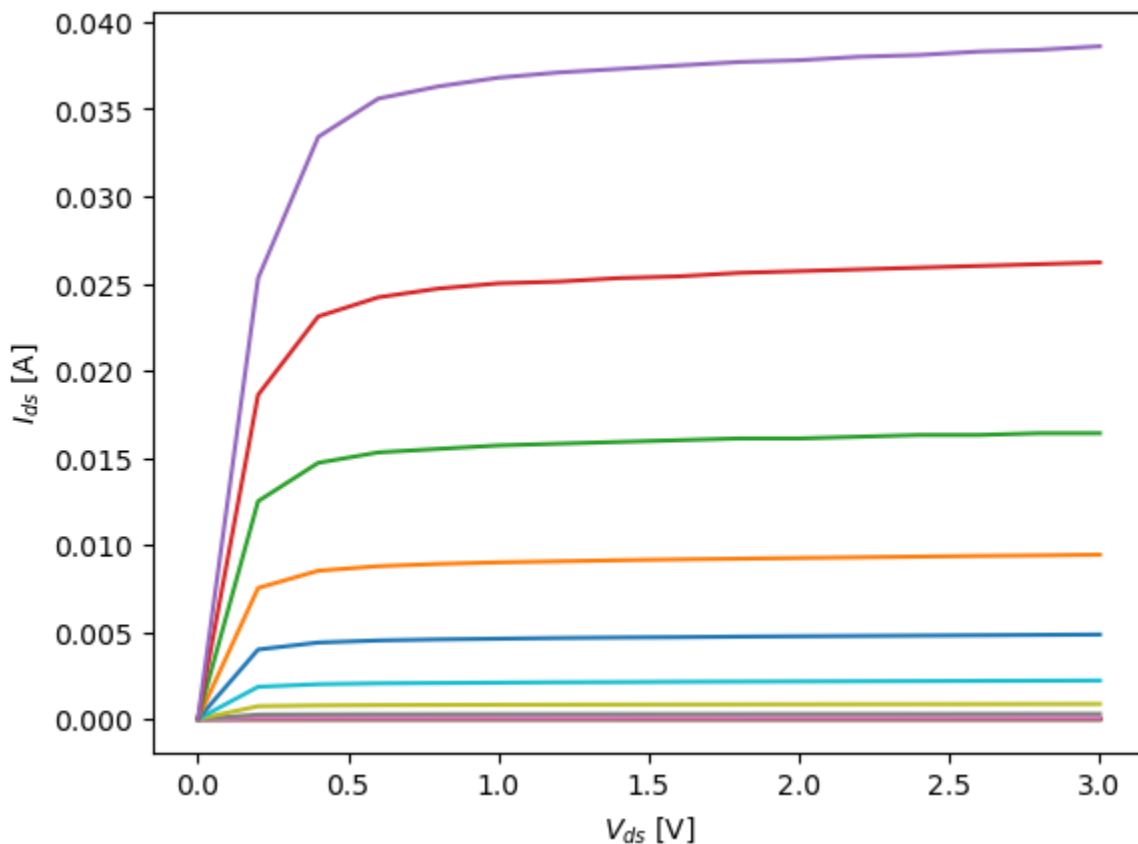

Plot I_D vs. V_{GS} .

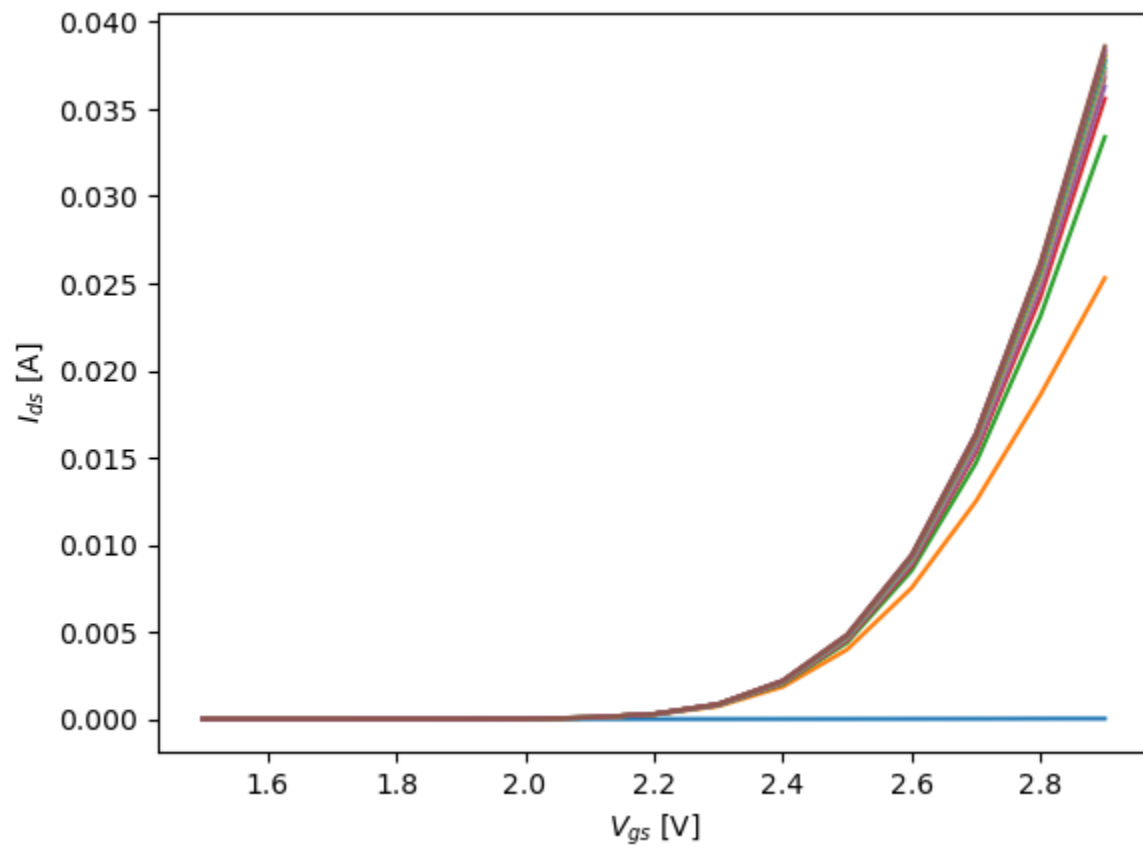




Plot g_m vs. V_{GS} .

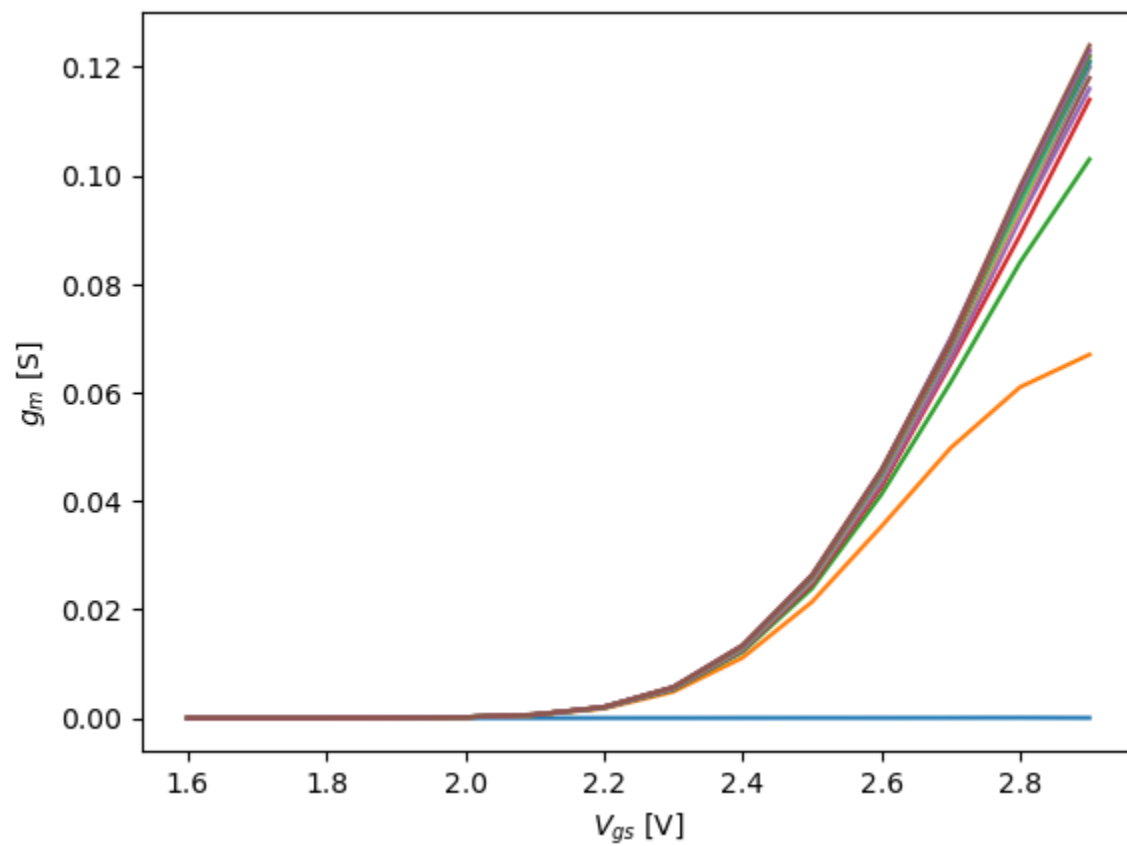

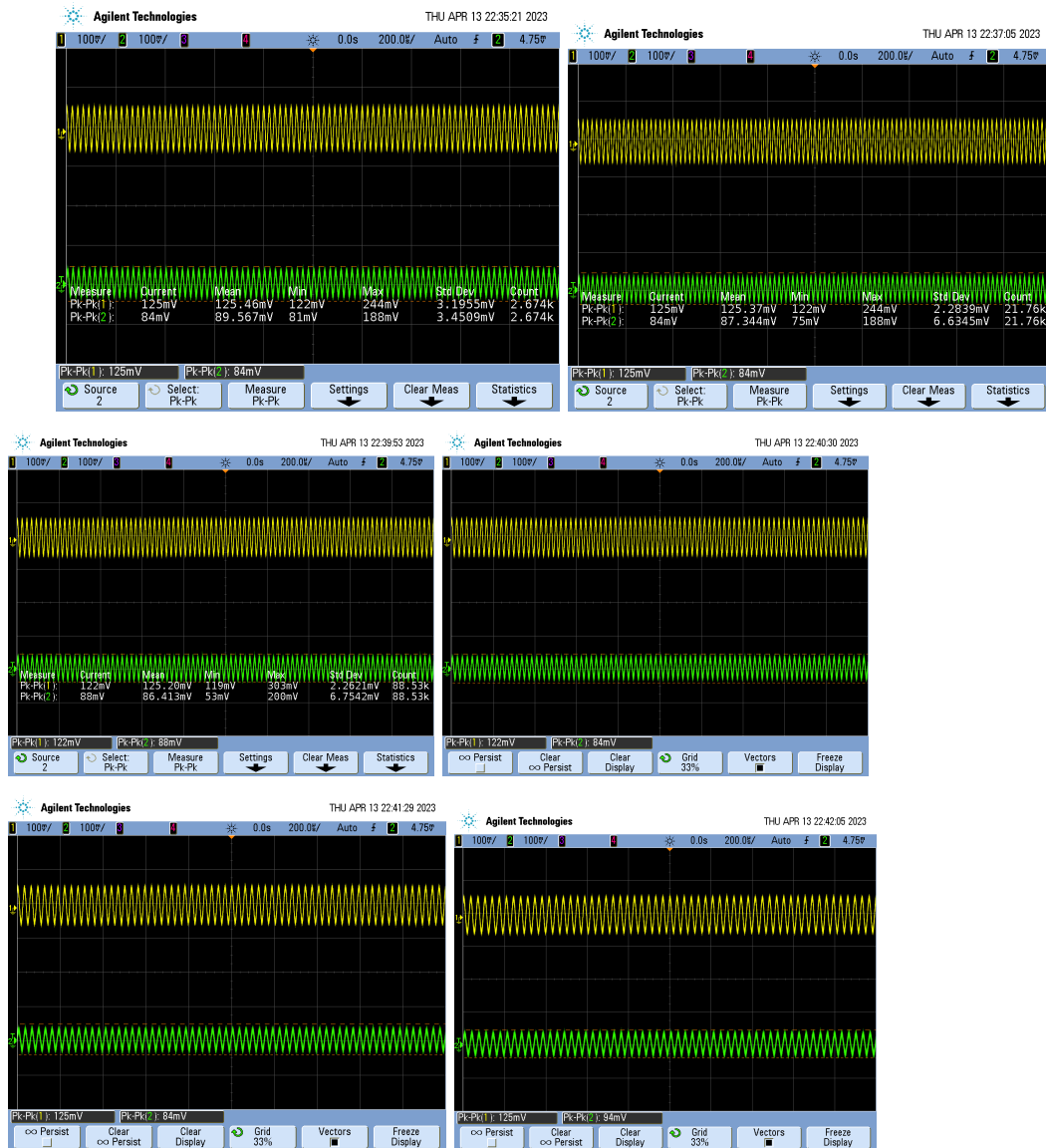
3.2. MOSFET Capacitance vs. Voltage

Oscilloscope traces (showing input and output) for $V_{gs} = 1.2V$ to $2.2V$ in $0.1V$ steps



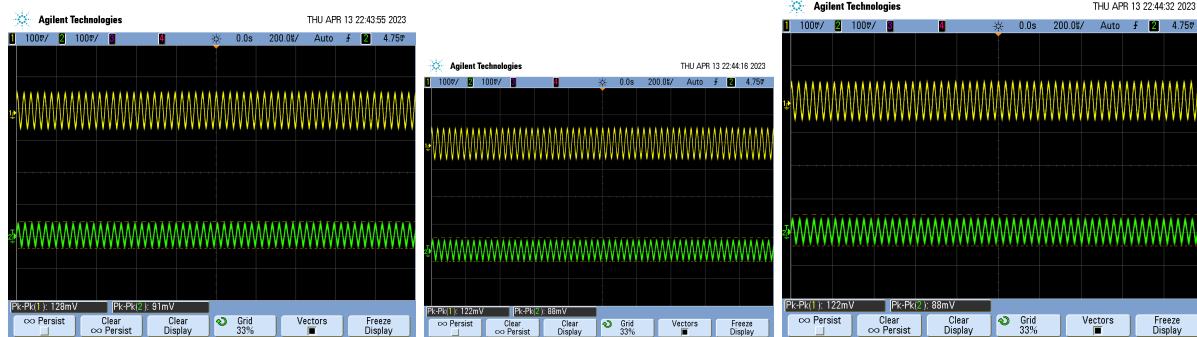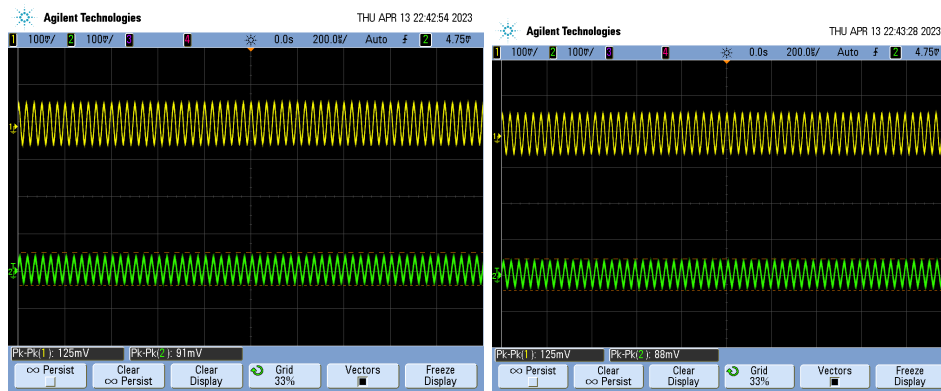


Parasitic Capacitance trace:

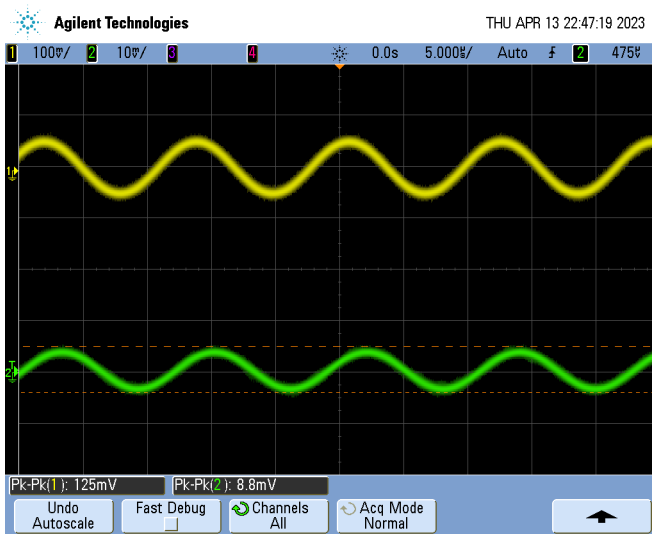

$$C_p = 19 \text{ pF}$$

Plot of V_{gs} vs. C_{gs} :

C_{gs} vs. V_{gs} (V)

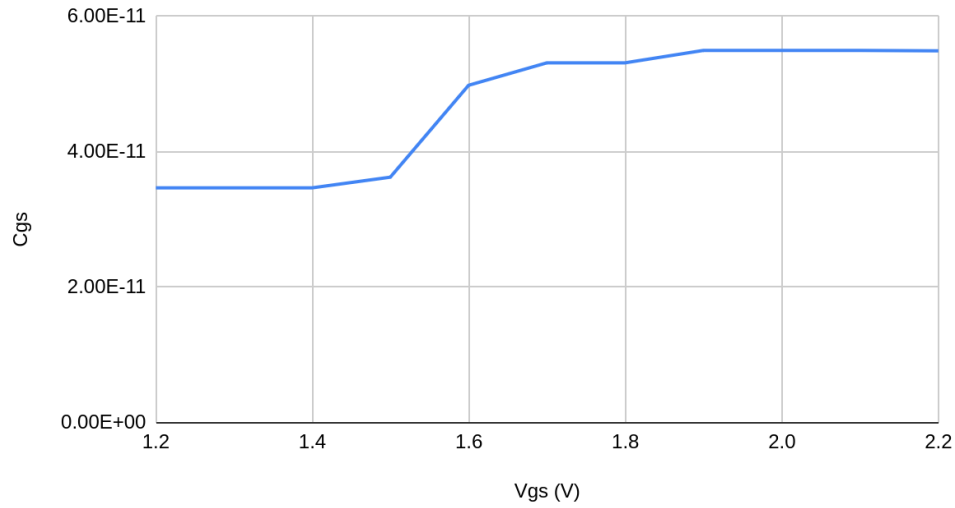

Why does the capacitance change with gate-source voltage? Explain it briefly.

The charge between the substrate and the metal of the MOSFET changes with gate-source voltage, so the MOSCAP's capacitance will change as a result.

3.3. Resistive Touch Sensor

Before touching

- $V_D = 1.2 \text{ V}$
- $V_G = 3 \text{ V}$
- $V_S = 0.43 \text{ V}$
- $I_D = 4.3 \text{ mA}$
- Region: Saturation

After touching

- $V_D = 1.7 \text{ V}$
- $V_G = 1 \text{ V}$
- $V_S = 0 \text{ V}$
- $I_D = 0 \text{ A}$
- Region: Cutoff