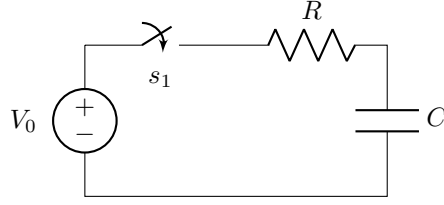


## EE 105 HW 01

## 1



The initial condition is  $V_C(t) = 0$ . Analyzing the current  $I_C(t)$ ,

$$\frac{V_0 - V_C(t)}{R} = C \frac{dV_C}{dt} \quad (1)$$

$$V_0 - V_C(t) = RC \frac{dV_C}{dt} \quad (2)$$

$$\frac{1}{V_0 - V_C(t)} = \frac{1}{RC} \frac{dt}{dV_C} \quad (3)$$

$$\int \frac{1}{V_0 - V_C(t)} dV_C = \int \frac{1}{RC} dt \quad (4)$$

$$-\ln |V_0 - V_C(t)| + C_0 = \frac{t}{RC} + C_1 \quad (5)$$

$$V_0 - V_C(t) = C_2 e^{-\frac{t}{RC}} \quad (6)$$

$$V_C(t) = V_0 - C_2 e^{-\frac{t}{RC}} \quad (7)$$

Solving for the initial condition,


$$0 = V_0 - C_2 \implies C_2 = V_0 \quad (8)$$

Thus, we have


$$V_C(t) = V_0(1 - e^{-\frac{t}{RC}}) \quad (9)$$

$$I_C(t) = C \frac{dV_C}{dt} = \frac{\cancel{V_0} - \cancel{V_0} + V_0 e^{-\frac{t}{RC}}}{R} = \frac{V_0}{R} e^{-\frac{t}{RC}} \quad (10)$$

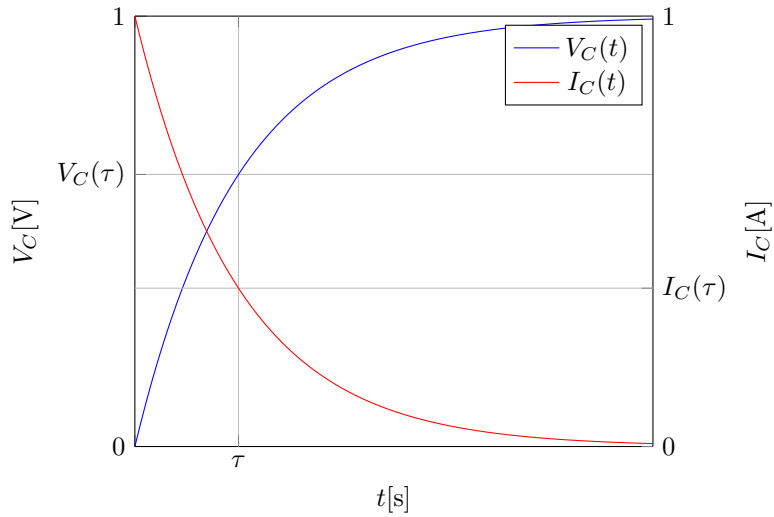Assuming  $V_0 = 1 \text{ V}$ ,  $R = 1 \Omega$ , and  $C = 1 \text{ F}$ ,



## 2

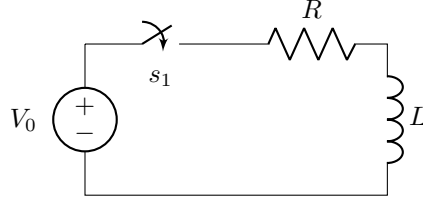

The initial condition is  $I_L(t) = 0$ . Analyzing the voltage loop including  $V_L(t)$ ,

$$V_0 - I_L(t)R - L \frac{dI_L}{dt} = 0 \quad (11)$$

$$\frac{V_0}{R} - I_L(t) = \frac{L}{R} \frac{dI_L}{dt} \quad (12)$$

$$\int \frac{1}{\frac{V_0}{R} - I_L(t)} dI_L = \int \frac{R}{L} dt \quad (13)$$

$$-\ln \left| \frac{V_0}{R} - I_L(t) \right| + C_0 = \frac{R}{L} t + C_1 \quad (14)$$

$$\frac{V_0}{R} - I_L(t) = C_2 e^{-\frac{R}{L} t} \quad (15)$$

$$I_L(t) = \frac{V_0}{R} - C_2 e^{-\frac{R}{L} t} \quad (16)$$

Solving for the initial condition,


$$0 = \frac{V_0}{R} - C_2 \implies C_2 = \frac{V_0}{R} \quad (17)$$

Thus, we have


$$I_L(t) = \frac{V_0}{R} (1 - e^{-\frac{R}{L} t}) \quad (18)$$

$$V_L(t) = \cancel{V_0} - \cancel{V_0} + V_0 e^{-\frac{R}{L} t} = V_0 e^{-\frac{R}{L} t} \quad (19)$$

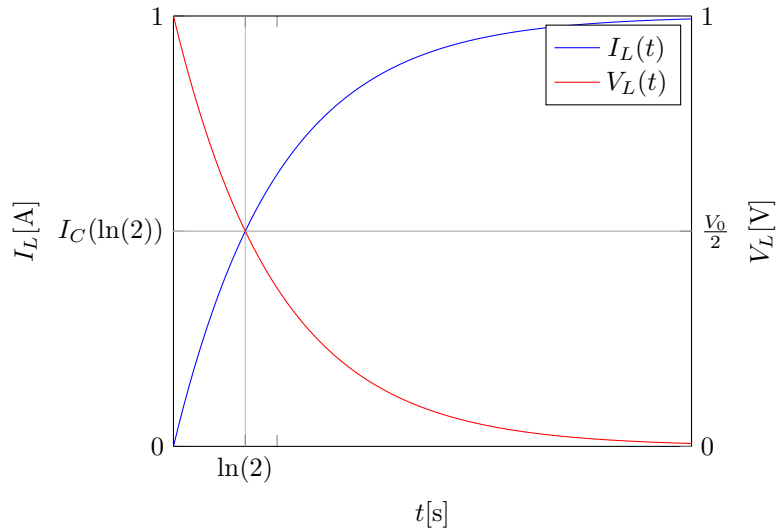Assuming  $V_0 = 1 \text{ V}$ ,  $R = 1 \Omega$ , and  $L = 1 \text{ H}$ ,



## 3

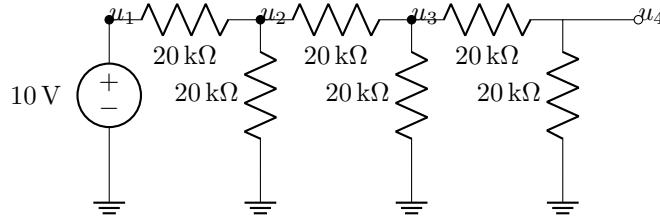

Using nodal voltage analysis, we obtain the following equations:


$$u_1 = 10 \text{ V} \quad (20)$$

$$u_1 = 3u_2 - u_3 \quad (21)$$

$$u_2 = 3u_3 - u_4 \quad (22)$$


$$u_3 = 2u_4 \quad (23)$$

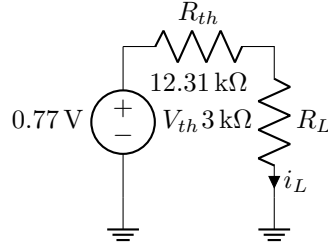Solving for these gives us  $u_4 = \frac{1}{13}10 \text{ V} \approx 0.77 \text{ V}$ . The Thévenin equivalent resistance is  $\frac{8}{13}20 \text{ k}\Omega \approx 12.31 \text{ k}\Omega$ . The equivalent circuit is thus



We find that  $i_L = \frac{V_{th}}{R_{th} + R_L} \approx 5.03 \times 10^{-5} \text{ A}$ .

## 4

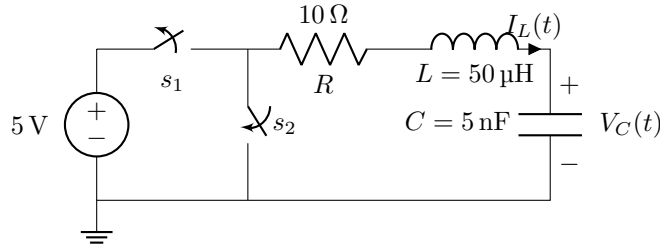

The initial conditions are  $V_C(0) = 5 \text{ V}$  and  $I_L(0) = 0 \text{ A}$ . Performing nodal voltage analysis at  $t \geq 0$ , we obtain the equations

$$I_L(t) = C \frac{dV_C}{dt} \quad (24)$$

$$-I_L(t)R - V_C(t) = L \frac{dI_L}{dt} \quad (25)$$

Let  $x_1(t) = V_C(t)$  and  $x_2(t) = I_L(t)$ . In state space form, we get

$$\frac{d}{dt} \mathbf{x}(t) = \begin{bmatrix} 0 & \frac{1}{C} \\ -\frac{1}{L} & -\frac{R}{L} \end{bmatrix} \mathbf{x}(t) = \underbrace{\begin{bmatrix} 0 & \frac{1}{5 \times 10^{-9}} \\ -\frac{1}{50 \times 10^{-6}} & -\frac{10}{50 \times 10^{-6}} \end{bmatrix}}_{\mathbf{A}} \mathbf{x}(t) \quad (26)$$

The eigenvalues are

$$\begin{vmatrix} -\lambda & 2 \times 10^8 \\ -2 \times 10^4 & -2 \times 10^5 - \lambda \end{vmatrix} = \lambda^2 + (2 \times 10^5)\lambda + (4 \times 10^{12}) = 0 \quad (27)$$

$$\implies \lambda = -10^5 \pm \sqrt{10^{10} - 4 \times 10^{12}} \quad (28)$$

$$= -10^5 \pm 10^5 \sqrt{1 - 4 \times 10^2} = -10^5 \pm 10^5 \sqrt{399}j \quad (29)$$

$$\approx -10^5 \pm (2 \times 10^6)j \quad (30)$$

The eigenvectors are

$$\mathbf{A} - \lambda_1 \mathbf{I} = \begin{bmatrix} 10^5 - 10^5 \sqrt{399}j & 2 \times 10^8 \\ -2 \times 10^4 & -2 \times 10^5 + 10^5 - 10^5 \sqrt{399}j \end{bmatrix} \quad (31)$$

$$= \begin{bmatrix} 10^5 - 10^5 \sqrt{399}j & 2 \times 10^8 \\ -2 \times 10^4 & -10^5 - 10^5 \sqrt{399}j \end{bmatrix} \quad (32)$$

$$R_1 \leftarrow \frac{R_1}{-\lambda_1} \implies \begin{bmatrix} 1 & 5 + 5\sqrt{399}j \\ -2 \times 10^4 & -10^5 - 10^5 \sqrt{399}j \end{bmatrix} \quad (33)$$

$$R_2 \leftarrow R_2 - (2 \times 10^4)R_1 \implies \begin{bmatrix} 1 & 5 + 5\sqrt{399}j \\ 0 & 0 \end{bmatrix} \implies \mathbf{v}_1 = \begin{bmatrix} -5 - 5\sqrt{399}j \\ 1 \end{bmatrix} \approx \begin{bmatrix} -5 - 100j \\ 1 \end{bmatrix} \quad (34)$$

$$\mathbf{A} - \lambda_2 \mathbf{I} = \begin{bmatrix} 10^5 + 10^5 \sqrt{399}j & 2 \times 10^8 \\ -2 \times 10^4 & -2 \times 10^5 + 10^5 + 10^5 \sqrt{399}j \end{bmatrix} \quad (35)$$

$$= \begin{bmatrix} 10^5 + 10^5 \sqrt{399}j & 2 \times 10^8 \\ -2 \times 10^4 & -10^5 + 10^5 \sqrt{399}j \end{bmatrix} \quad (36)$$

$$R_1 \leftarrow \frac{R_1}{-\lambda_2} \implies \begin{bmatrix} 1 & 5 - 5\sqrt{399}j \\ -2 \times 10^4 & -10^5 + 10^5 \sqrt{399}j \end{bmatrix} \quad (37)$$

$$R_2 \leftarrow R_2 + (2 \times 10^4)R_1 \implies \begin{bmatrix} 1 & 5 - 5\sqrt{399}j \\ 0 & 0 \end{bmatrix} \implies \mathbf{v}_1 = \begin{bmatrix} -5 + 5\sqrt{399}j \\ 1 \end{bmatrix} \approx \begin{bmatrix} -5 + 100j \\ 1 \end{bmatrix} \quad (38)$$

$$\implies \mathbf{V} \approx \begin{bmatrix} -5 - 100j & -5 + 100j \\ 1 & 1 \end{bmatrix} \quad (39)$$

$$\mathbf{V}^{-1} \approx \frac{1}{200} \begin{bmatrix} j & 100 + 5j \\ -j & 100 - 5j \end{bmatrix} \quad (40)$$

The transformed initial condition is

$$\mathbf{z}(0) = \mathbf{V}^{-1} \begin{bmatrix} 5 \\ 0 \end{bmatrix} \approx \begin{bmatrix} \frac{j}{40} \\ -\frac{j}{40} \end{bmatrix} \quad (41)$$

Solving the diagonalized system, we have

$$\frac{d}{dt} \mathbf{z}(t) = \begin{bmatrix} \lambda_1 & 0 \\ 0 & \lambda_2 \end{bmatrix} \mathbf{z}(t) \implies \mathbf{z}(t) \approx \begin{bmatrix} \frac{j}{40} e^{(-10^5 + (2 \times 10^6)j)t} \\ -\frac{j}{40} e^{(-10^5 - (2 \times 10^6)j)t} \end{bmatrix} \quad (42)$$

The final equation is thus

$$\mathbf{x}(t) = \mathbf{V}\mathbf{z}(t) \approx \frac{j}{40} \begin{bmatrix} -5 - 100j & -5 + 100j \\ 1 & 1 \end{bmatrix} \begin{bmatrix} e^{(-10^5 + (2 \times 10^6)j)t} \\ -e^{(-10^5 - (2 \times 10^6)j)t} \end{bmatrix} \quad (43)$$

$$= \frac{j}{40} \begin{bmatrix} -5(e^{(-10^5 + (2 \times 10^6)j)t} - e^{(-10^5 - (2 \times 10^6)j)t}) \\ e^{(-10^5 + (2 \times 10^6)j)t} - e^{(-10^5 - (2 \times 10^6)j)t} \end{bmatrix} \quad (44)$$

$$= \frac{je^{-10^5 t}}{40} \begin{bmatrix} -5(e^{(2 \times 10^6)jt} - e^{(-2 \times 10^6)jt}) - 100j(e^{(2 \times 10^6)jt} + e^{(-2 \times 10^6)jt}) \\ e^{(2 \times 10^6)jt} - e^{(-2 \times 10^6)jt} \end{bmatrix} \quad (45)$$

$$= \frac{je^{-10^5 t}}{40} \begin{bmatrix} -10j \sin((2 \times 10^6)t) - 200j \cos((2 \times 10^6)t) \\ 2j \sin((2 \times 10^6)t) \end{bmatrix} \quad (46)$$

$$= \frac{e^{-10^5 t}}{40} \begin{bmatrix} 10 \sin((2 \times 10^6)t) + 200 \cos((2 \times 10^6)t) \\ -2 \sin((2 \times 10^6)t) \end{bmatrix} \quad (47)$$